

CS221 HW_Lab Report

Name : Kartik Disawal

Roll number: 2003119

Branch : Computer Science and Engineering

Submission Date : 24-05-2022




Submitted to :

Sharad sir


Question : Synthesize the given behavioural code and plot the 'number of slices' used vs 'No. of registers' and 'the minimum clock cycle period' in ns vs 'No. of registers' (change the parameter for No. of registers {NREG=16, 32, 64}). Here we can keep the bit-width of each register (DSIZE parameter) to be constant (for example DSIZE=32).

| No. of registers (NREG) | Bit-width (DSIZE) | No. of register slices used | No. of LUT slices used | Min clock period in ns |
|-------------------------|-------------------|-----------------------------|------------------------|------------------------|
| 4 | 32 | 128 | 186 | 3.899 |
| 8 | 32 | 256 | 302 | 4.345 |
| 16 | 32 | 512 | 502 | 4.546 |
| 32 | 32 | 1024 | 900 | 6.456 |
| 64 | 32 | 1024 | 900 | 7.786 |

 


Question : Synthesize the given behavioralcode and plot the number of slices used vs bit-width of the register (DSIZE) and delay in ns vs bit-width of the register (change the parameter for bit-width of the registers {DSIZE=16, 32, 64}). Here we can keep the number of registers (NREGparameter) to be constant (for example NREG=32) and thus ASIZE will be a constant =5.

| No. of registers (NREG) | Bit-width (DSIZE) | No. of register slices used | No. of LUT slices used | Min clock period in ns |
|-------------------------|-------------------|-----------------------------|------------------------|------------------------|
| 32 | 4 | 128 | 144 | 6.756 |
| 32 | 8 | 256 | 252 | 6.998 |
| 32 | 16 | 512 | 468 | 6.435 |
| 32 | 32 | 1024 | 900 | 6.363 |
| 32 | 64 | 2048 | 1764 | IO port insuffienct |

 

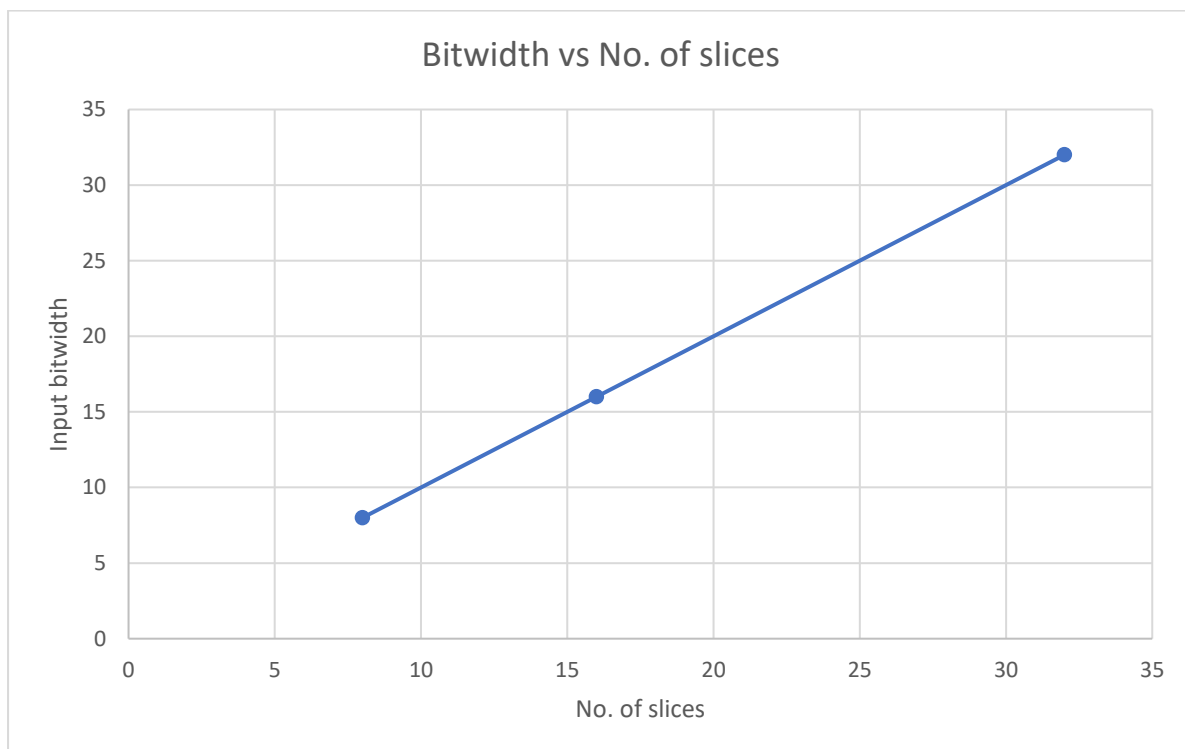Question : You are given the Verilog code as well as the test bench for ALU. You have to test whether the ALU gives correct results. B. You need to set the input bit-width to 8, 16 and 32 (one by one) and find out the number of slices used. You need to plot area (vs) bit-width as well as delay (vs) bit-width for the ALU module. In FPGA you cannot find area directly so instead of area you can take number of slices, which would be considered proportional to the area.



| Input bitwidth | No. of registers(NREG) | No. of slices | Min clock period in ns |
|----------------|------------------------|---------------|------------------------|
| 8 | 32 | 8 | 8.234 |
| 16 | 32 | 16 | 8.654 |
| 32 | 32 | 32 | 11.765 |